



Reference	Component	Value	Quantity
V1	DC power supply (battery)	125V	1
R1	Resistor	20 Ω	1
R2	Resistor	100 Ω	1
R3	Resistor	50 Ω	1

Schematic	Schematic2 - CIRCUIT B		Create at	2026-10-03
			Update at	2026-10-03
Board			Page	Circuit b - Parallel
Drawn		Lab Exercise Schematics with ESP32 Part B 1		
Reviewed				
		Version	Size	Page 1 Total 1
		V1.0	A4	EasyEDA.com